

CPU设计汇报

汇报人：智能1601 201608010312 张宁

目录

1

设计要求

2

设计思想

3

代码实现



01

设计要求



相对简单CPU的规格说明

1. 64K字节的存储器，每个存储单元8位宽。

地址引脚A[15..0]

数据引脚D[7..0]


2. CPU的三个内部寄存器

◆ 8位累加器AC：接受任何算术或者逻辑运算的结果，并为使用两个操作数的算术或者逻辑操作指令提供一个操作数。

◆ 寄存器R：一个8位通用寄存器。它为所有的双操作数算术和逻辑运算指令提供第二个操作数。它也可以用来暂时存放累加器马上要用到的数据。（减少存储器访问次数提高CPU的性能）

◆ 零标志位Z：每次执行算术运算或者逻辑运算的时候，它都将被置位。



 


寄存器

- ◆ 16位的地址寄存器AR：通过引脚A[15..0]向存储器提供地址。
- ◆ 16位的程序计数器PC：存放的是将要执行的下一条指令的地址，或者指令需要的下一个操作数的地址。
- ◆ 8位的数据寄存器DR：通过D[7..0]从存储器中接收指令和数据并且向存储器传送数据。
- ◆ 8位的指令寄存器IR：存放的是从存储器中取出来的操作码。
- ◆ 8位的临时寄存器TR：在指令执行过程中，临时存储数据。（程序员不能访问）



指令集结构

指令	指令码	操作
NOP	0000 0000	无
LDAC	0000 0001 Γ	$AC \leftarrow M[\Gamma]$
STAC	0000 0010 Γ	$M[\Gamma] \leftarrow AC$
MVAC	0000 0011	$R \leftarrow AC$
MOVR	0000 0100	$AC \leftarrow R$
JUMP	0000 0101 Γ	GOTO Γ
JMPZ	0000 0110 Γ	IF ($Z=1$) THEN GOTO Γ
JPNZ	0000 0111 Γ	IF ($Z=0$) THEN GOTO Γ

 

指令集结构

ADD	0000 1000	$AC \leftarrow AC + R$, IF $(AC + R = 0)$ THEN $Z \leftarrow 1$ ELSE $Z \leftarrow 0$
SUB	0000 1001	$AC \leftarrow AC - R$, IF $(AC - R = 0)$ THEN $Z \leftarrow 1$ ELSE $Z \leftarrow 0$
INAC	0000 1010	$AC \leftarrow AC + 1$, IF $(AC + 1 = 0)$ THEN $Z \leftarrow 1$ ELSE $Z \leftarrow 0$
CLAC	0000 1011	$AC \leftarrow 0a$, $Z \leftarrow 1$
AND	0000 1100	$AC \leftarrow AC \wedge R$, IF $(AC \wedge R = 0)$ THEN $Z \leftarrow 1$ ELSE $Z \leftarrow 0$
OR	0000 1101	$AC \leftarrow AC \vee R$, IF $(AC \vee R = 0)$ THEN $Z \leftarrow 1$ ELSE $Z \leftarrow 0$
XOR	0000 1110	$AC \leftarrow AC \oplus R$, IF $(AC \oplus R = 0)$ THEN $Z \leftarrow 1$ ELSE $Z \leftarrow 0$
NOT	0000 1111	$AC \leftarrow AC'$, IF $(AC' = 0)$ THEN $Z \leftarrow 1$ ELSE $Z \leftarrow 0$



指令执行具体过程

执行指令

LDAC指令

- LDAC是一条多字指令。
- 它包含三个字：
- 操作码 地址的低半部分 地址的高半部分
- 功能：从存储器中获得地址，然后从存储器中获得数据，并把数据装载到累加器中。

F1: $AR \leftarrow PC$

F2: $DR \leftarrow M, PC \leftarrow PC + 1$

F3: $IR \leftarrow DR, AR \leftarrow PC$


L1: $DR \leftarrow M, PC \leftarrow PC + 1, AR \leftarrow AR + 1$

L2: $TR \leftarrow DR, DR \leftarrow M, PC \leftarrow PC + 1$

L3: $AR \leftarrow DR, TR$

L4: $DR \leftarrow M$

L5: $AC \leftarrow DR$

 

JUMP指令

JUMP1: $DR \leftarrow M, AR \leftarrow AR + 1$

JUMP2: $TR \leftarrow DR, DR \leftarrow M$

JUMP3: $PC \leftarrow DR, TR$

JMPZ指令的状态:

JMPZY1: $DR \leftarrow M, AR \leftarrow AR + 1$

JMPZY2: $TR \leftarrow DR, DR \leftarrow M$

JMPZY3: $PC \leftarrow DR, TR$

JMPZN1: $PC \leftarrow PC + 1$

JMPZN2: $PC \leftarrow PC + 1$

其余的指令都是在一个状态内完成的。



- 1、明确CPU的功能、目的和基本规格
- 2、设计指令集结构
- 3、取指令、译码（画出状态图）
- 4、执行指令（明确指令的状态）
- 5、创建数据通路
- 6、设计ALU等
- 7、设计控制单元
- 8、产生CPU的状态



设计思想



环境: Quartus II 9.0

仿真: Quartus 下进行波形仿真

- 根据状态图对指令执行状态译码
 - 其中LDAC、STAC需要5个状态完成，JUMP需要3个状态完成，其余均一个状态完成。


```
constant ldac1:      std_logic_vector(5 downto 0) := "001110";  
constant ldac2:      std_logic_vector(5 downto 0) := "001111";  
constant ldac3:      std_logic_vector(5 downto 0) := "010000";  
constant ldac4:      std_logic_vector(5 downto 0) := "010001";  
constant ldac5:      std_logic_vector(5 downto 0) := "010010";
```

- 时钟上升沿时，根据指令更新寄存器的值
- 产生下一状态的进程（根据当前指令产生下一状态）
- 对每个状态译码（信号如何变化）



在mem.vhd文件中，验证 $1+2+\dots+n$ 。（没有过多改动）

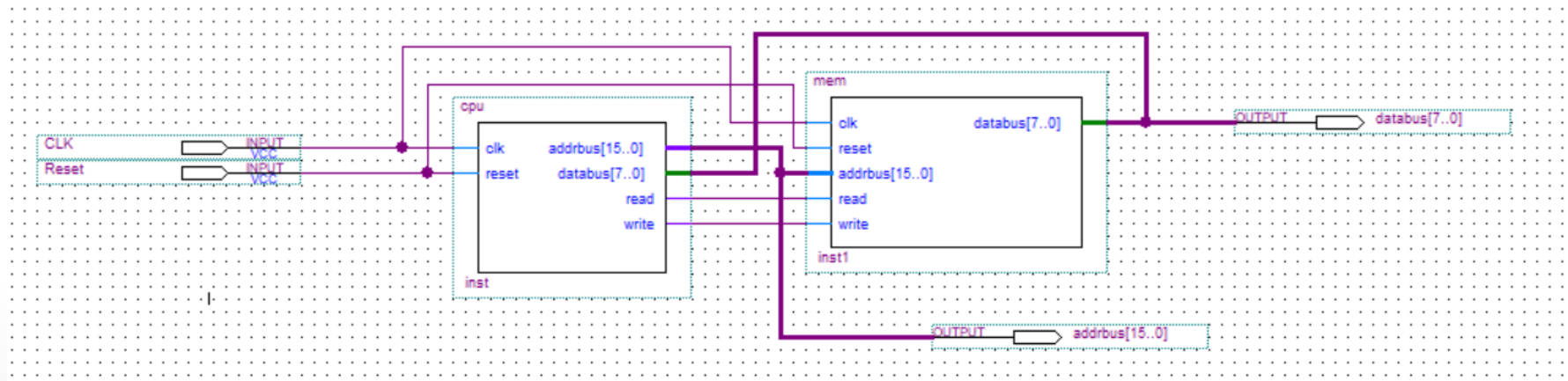
在comp工程中，把cpu.vhd、rsisa.vhd、mem.vhd三个文件添加进来，通过画图的方式连接。





03

代码实现

 

cpu.vhd:

```
signal pc: std_logic_vector(15 downto 0);
signal ac: std_logic_vector(7 downto 0);
signal r: std_logic_vector(7 downto 0);
signal ar: std_logic_vector(15 downto 0);
signal ir: std_logic_vector(7 downto 0);
signal dr: std_logic_vector(7 downto 0);
signal tr: std_logic_vector(7 downto 0);
signal z: std_logic;

signal arinc: std_logic;
signal writel: std_logic;
signal pcbus: std_logic;
signal membus: std_logic;
signal rbus: std_logic;
signal acbus: std_logic;
signal trbus: std_logic;
signal drbus: std_logic;
signal pload: std_logic;
signal arload: std_logic;
signal drload: std_logic;
signal irload: std_logic;
signal acload: std_logic;
signal rload: std_logic;
signal trload: std_logic;
signal nextpc: std_logic_vector(15 downto 0);
signal state: std_logic_vector(5 downto 0);
signal nextstate: std_logic_vector(5 downto 0)

constant fetch1: std_logic_vector(5 downto 0) := "000000";
constant fetch2: std_logic_vector(5 downto 0) := "000001";
constant fetch3: std_logic_vector(5 downto 0) := "000010";

constant clacl: std_logic_vector(5 downto 0) := "000100";
constant incac1: std_logic_vector(5 downto 0) := "000101";
constant add1: std_logic_vector(5 downto 0) := "000110";
constant sub1: std_logic_vector(5 downto 0) := "000111";
constant and1: std_logic_vector(5 downto 0) := "001000";
constant or1: std_logic_vector(5 downto 0) := "001001";
constant xor1: std_logic_vector(5 downto 0) := "001010";
constant not1: std_logic_vector(5 downto 0) := "001011";
constant mvac1: std_logic_vector(5 downto 0) := "001100";
constant movr1: std_logic_vector(5 downto 0) := "001101";
constant ldac1: std_logic_vector(5 downto 0) := "001110";
constant ldac2: std_logic_vector(5 downto 0) := "001111";
constant ldac3: std_logic_vector(5 downto 0) := "010000";
constant ldac4: std_logic_vector(5 downto 0) := "010001";
constant ldac5: std_logic_vector(5 downto 0) := "010010";
constant stac1: std_logic_vector(5 downto 0) := "010011";
constant stac2: std_logic_vector(5 downto 0) := "010100";
constant stac3: std_logic_vector(5 downto 0) := "010101";
constant stac4: std_logic_vector(5 downto 0) := "010110";
constant stac5: std_logic_vector(5 downto 0) := "010111";
```




cpu.vhd:

```
-- update pc, state and other registers
update_regs: process(clk)
if(arload='1') then ar<=busl6;
end if;
if(drload='1') then dr<=busl6(7 downto 0);
end if;
if(irload='1') then ir<=dr;
end if;
for_nextstate: process(state, ir, z)
begin

    if(state=fetch1) then nextstate<=fetch2;
    elsif(state=fetch2) then nextstate<=fetch3;
    elsif(state=fetch3) then
        if(dr=RSLCLAC) then nextstate<=clacl;
        elsif(dr=RSINAC) then nextstate<=incac;
        elsif(dr=RSADD) then nextstate<=addl;
        elsif(dr=RSSUB) then nextstate<=subl;
        elsif(dr=RSAND) then nextstate<=andl;
        elsif(dr=RSOR) then nextstate<=orl;
        elsif(dr=RSXOR) then nextstate<=xorl;
        elsif(dr=RSNOT) then nextstate<=notl;
        elsif(dr=RSMVAC) then nextstate<=mvac;
        elsif(dr=RSMOVR) then nextstate<=movr;
        elsif(dr=RSLDAC) then nextstate<=ldacl;
        elsif(dr=RSSTAC) then nextstate<=stacl;
        elsif(dr=RSJUMP) then nextstate<=jumpl;
```

```
-- generate control signals for each state
gen_controls: process(state)
begin
    if(state=fetch1) then
        arload<='1';
        pcbus<='1';
        pcinc<='0';
        drload<='0';
        membus<='0';
        irload<='0';
        acreset<='0';
        acinc<='0';
        rbus<='0';
        s<="0000";acload<='0';
        rload<='0';acbus<='0';
        arinc<='0';trbus<='0';
        drbus<='0';trload<='0';
        read<='0';writel<='0';
        write<='0';pcload<='0';
```




mem.vhd


```
architecture mem_behav of mem is
    signal addr: std_logic_vector(15 downto 0);

    type memtype is array(natural range<>) of std_logic_vector(7 downto 0);
    constant total_addr : integer := 29;
    constant i_addr : integer := 30;
    constant n_addr : integer := 31;
    constant loop_addr : integer := 7;
```

```
2 => std_logic_vector(to_unsigned(total_addr, 8)),
3 => X"00",
4 => RSSTAC, --i=0
5 => std_logic_vector(to_unsigned(i_addr, 8)),
6 => X"00",
7 => RSLDAC, -- loop |
8 => std_logic_vector(to_unsigned(i_addr, 8)),
9 => X"00",
10 => RSINAC,
11 => RSSTAC,
12 => std_logic_vector(to_unsigned(i_addr, 8)),
13 => X"00",
14 => RSMVAC,
15 => RSLDAC,
16 => std_logic_vector(to_unsigned(total_addr, 8)),
17 => X"00",
18 => RSADD, --ac=ac+r
19 => RSSTAC,
20 => std_logic_vector(to_unsigned(total_addr, 8)),
21 => X"00",
22 => RSLDAC,
23 => std_logic_vector(to_unsigned(n_addr, 8)),
24 => X"00",
25 => RSSUB,
26 => RSJPNZ,
27 => std_logic_vector(to_unsigned(loop_addr, 8)),
28 => X"00",
29 => X"00", -- total
30 => X"00", -- i
31 => "00000101", -- n
```




仿真结果

 



仿真结果

 

指令	1st Loop	2nd Loop	3rd Loop	4th Loop	5th Loop
CLAC	AC=0				
STAC total	total=0				
STAC i	i=0				
LDAC i	AC=0	AC=1	AC=2	AC=3	AC=4
INAC	AC=1	AC=2	AC=3	AC=4	AC=5
STAC i	i=1	i=2	i=3	i=4	i=5
MVAC	R=1	R=2	R=3	R=4	R=5
LDAC total	AC=0	AC=1	AC=3	AC=6	AC=10
ADD	AC=1	AC=3	AC=6	AC=10	AC=15
STAC total	total=1	total=3	total=6	total=10	total=15
LDAC n	AC=5	AC=5	AC=5	AC=5	AC=5
SUB	AC=4, Z=0	AC=3, Z=0	AC=2, Z=0	AC=1, Z=0	AC=0, Z=0
JPNZ Loop	JUMP	JUMP	JUMP	JUMP	NO_JUMP



THANKS!