 


相对简单CPU的设计

201608010627 任小禹


目录



CPU设计概述



遇到的问题及分析

 

测试结果




第一部分

Part One

CPU设计概述

CPU设计概述

- 测试环境：Quartus II, 四个vhdl文件

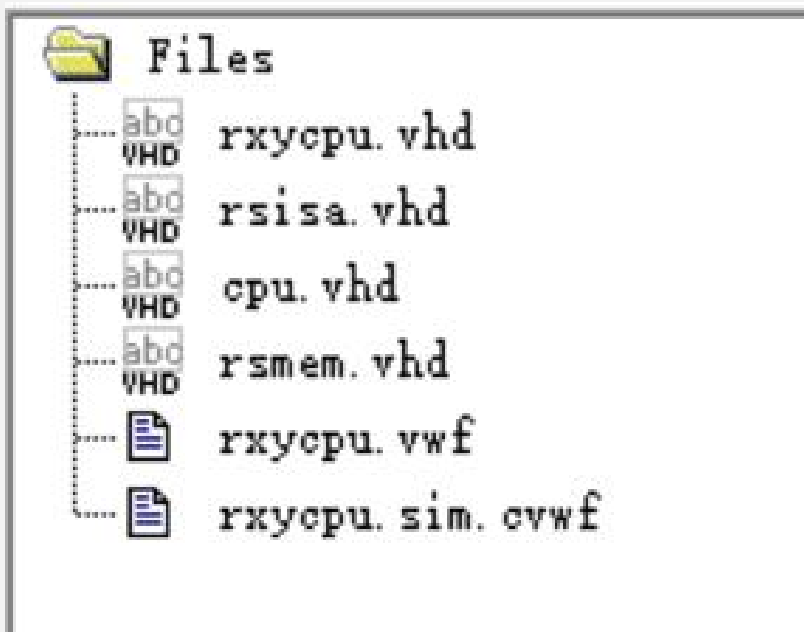

- 将CPU模块和内存连接起来
- 将我们CPU的指令集打包成库，方便调用
- CPU的具体实现
- 内存读写的实现及输入激励


CPU设计概述

- 指令执行过程分为取指、译码、执行三个阶段
- 取指包括四个状态:
FETCH1, FETCH2, FETCH3, FETCH4
 - FETCH1: $AR \leftarrow PC$
 - FETCH2: $DR \leftarrow M, PC \leftarrow PC + 1$
 - FETCH3: $IR \leftarrow DR,$
 - FETCH4: $AR \leftarrow PC$
- 译码体现为从FETCH4状态到各指令执行状态序列的第一个状态
- 这里将取分为四个阶段是因为防止还有译码成功, 状态就已经改变

CPU具体实现主要是CPU控制单元的设计


- 硬连线控制
 - 时序逻辑和组合逻辑产生控制信号
- 微程序控制
 - 存储器查表输出控制信号

我们采用硬连线控制

 

CPU设计概述

- 我们采用硬连线控制，列出整个CPU的状态图

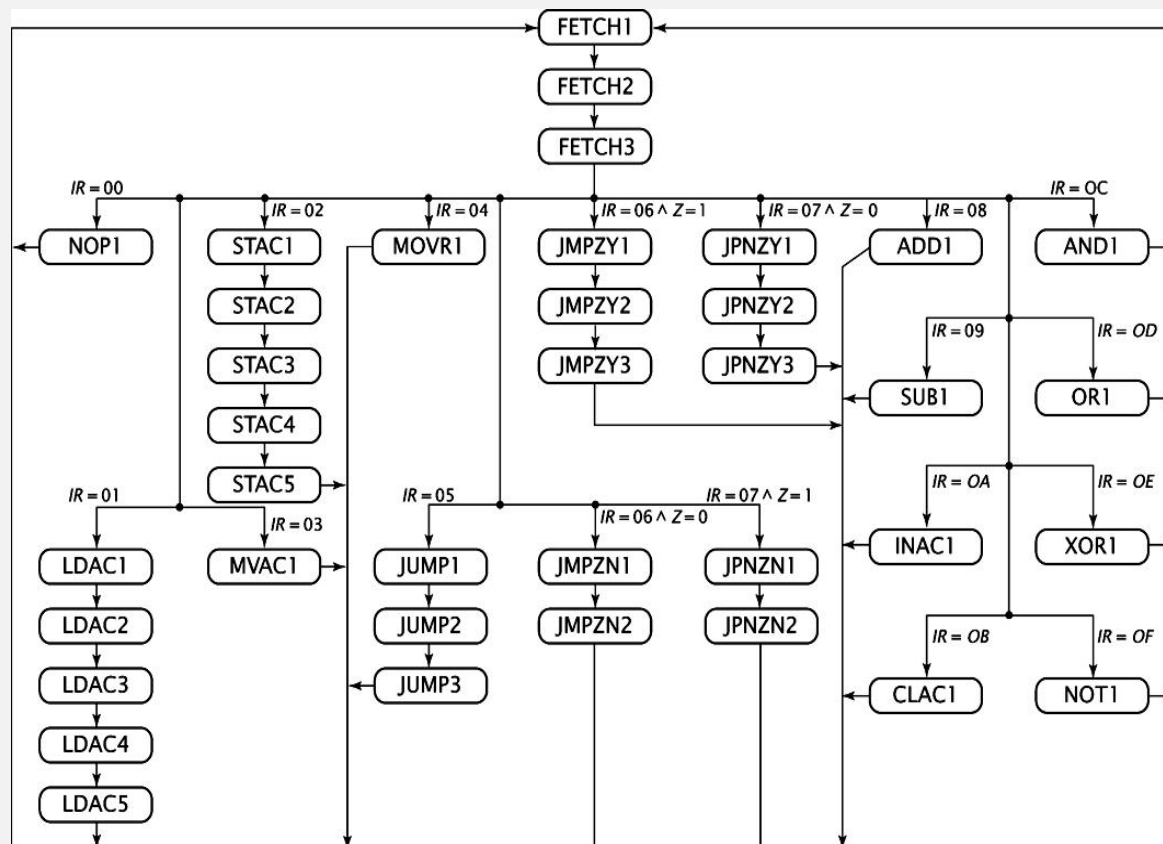

```
-- generate control signals for each state
for nextstate: process(state, ir, z)
```


- 相当于计数器，产生下一状态

```
-- generate control signals for each state
gen controls: process(state)
```

- 相当于译码器和组合逻辑，根据当前状态产生控制信号

CPU设计概述

- 不用vhdl的元件例化语句，也可以用原理图连线的方法实现

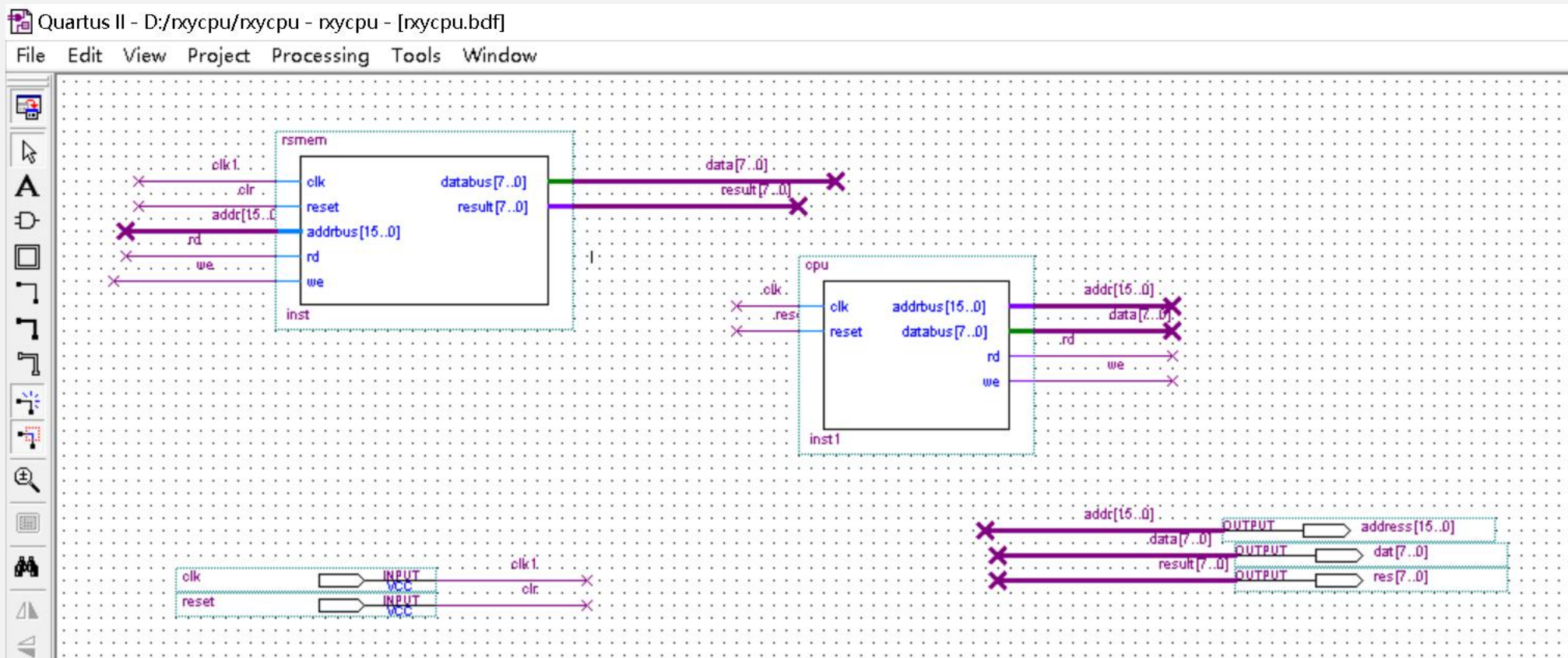







第二部分

Part One


遇到的问题及分析

遇到问题及分析1/3

Type	Message
	Error: Top-level design entity "rxycpu" is undefined
 	Error: Quartus II Analysis & Synthesis was unsuccessful. 1 error, 0 warnings
	Error: Quartus II Full Compilation was unsuccessful. 3 errors, 0 warnings

- quartus顶层文件名必须和工程名保持一致

遇到问题及分析 2/3

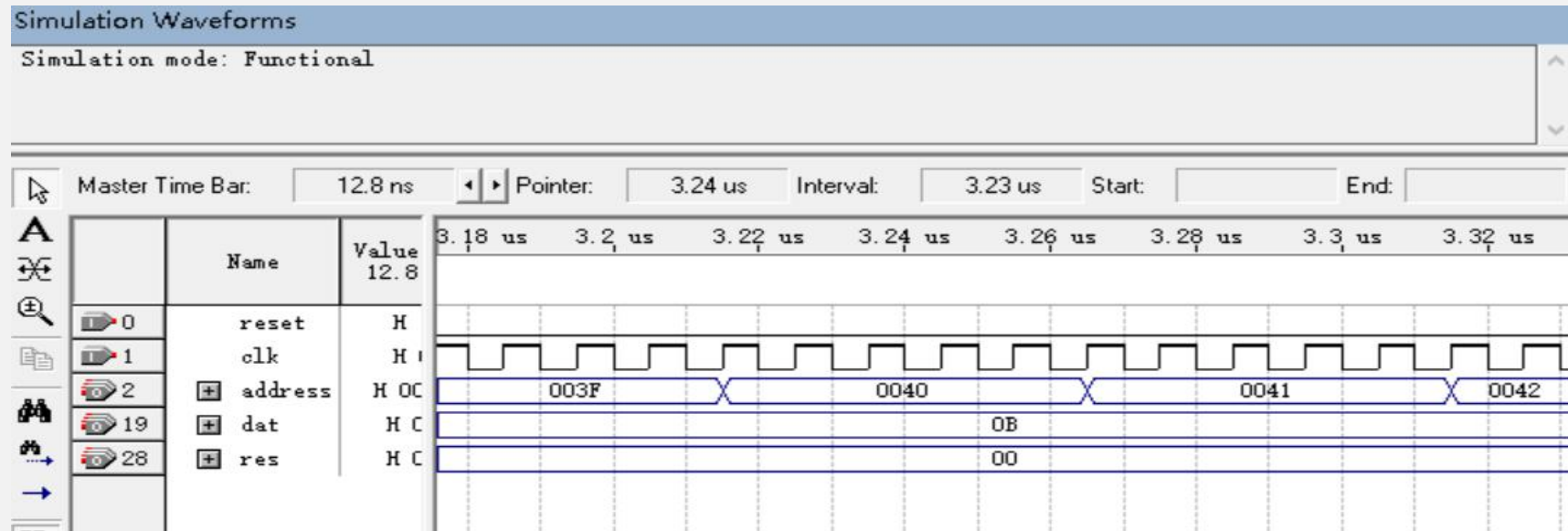


- 数据线数据一直不变，分析原因，可能是元件连接出错

遇到问题及分析 2/3

```
SIGNAL  addr :  STD_LOGIC_VECTOR(15 DOWNT0 0);  
SIGNAL  clk1 :  STD_LOGIC;  
SIGNAL  clr :  STD_LOGIC;  
SIGNAL  data :  STD_LOGIC_VECTOR(7 DOWNT0 0);  
SIGNAL  rd :  STD_LOGIC;  
SIGNAL  result :  STD_LOGIC_VECTOR(7 DOWNT0 0);  
SIGNAL  we :  STD_LOGIC;
```

- 元件连接的文件出错，我编写的元件例化语句有问题
- clk和reset均为输入信号，可以直接通过元件例化语句映射，无需中间信号变量

遇到问题及分析3/3

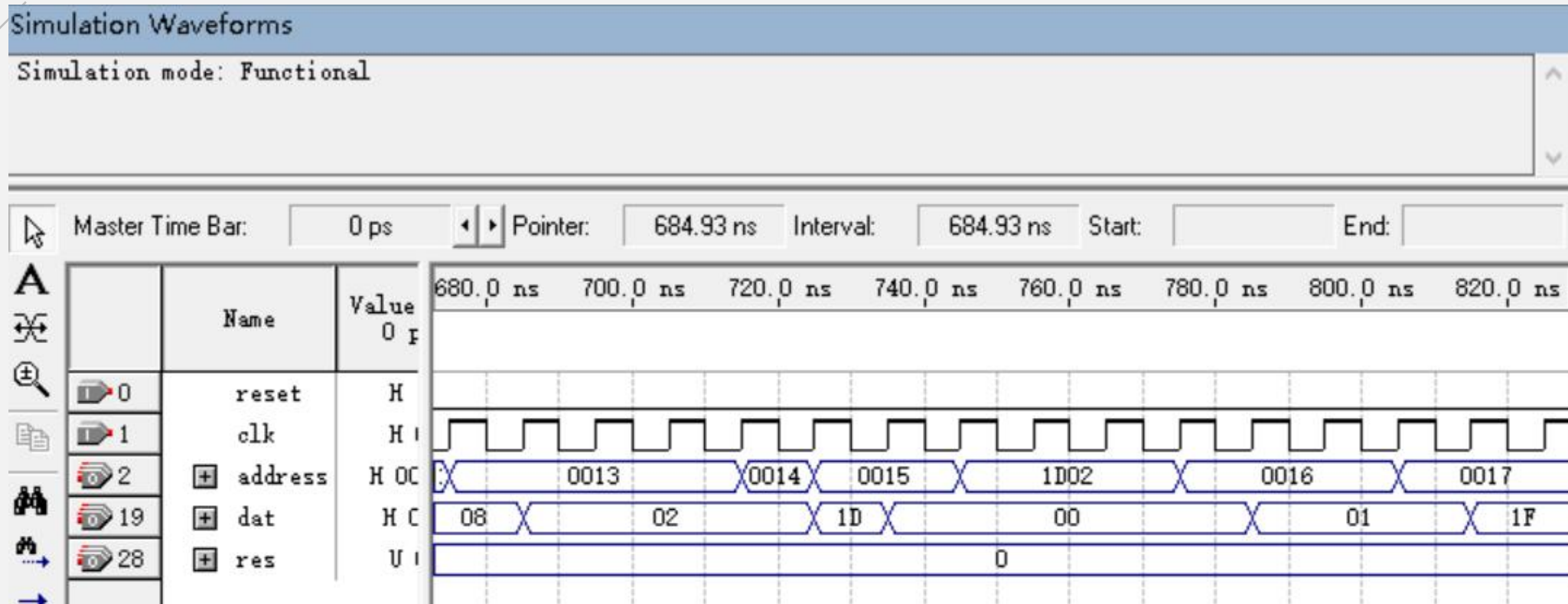

- 数据线有了数据一直不变，但是输出的total值一直为0

遇到问题及分析

```
yncram:memdata_rtl_0|altsyncram_aril:auto_generated|ram_blockla0" assumed to occur on falling edge of input clock  
yncram:memdata_rtl_0|altsyncram_aril:auto_generated|ram_blockla1" assumed to occur on falling edge of input clock  
yncram:memdata_rtl_0|altsyncram_aril:auto_generated|ram_blockla2" assumed to occur on falling edge of input clock  
yncram:memdata_rtl_0|altsyncram_aril:auto_generated|ram_blockla3" assumed to occur on falling edge of input clock  
yncram:memdata_rtl_0|altsyncram_aril:auto_generated|ram_blockla4" assumed to occur on falling edge of input clock  
yncram:memdata_rtl_0|altsyncram_aril:auto_generated|ram_blockla5" assumed to occur on falling edge of input clock  
yncram:memdata_rtl_0|altsyncram_aril:auto_generated|ram_blockla6" assumed to occur on falling edge of input clock  
yncram:memdata_rtl_0|altsyncram_aril:auto_generated|ram_blockla7" assumed to occur on falling edge of input clock
```

```
for_clk : process(clk)  
begin  
    if(rising_edge(clk)) then  
        if(reset='1') then  
            addr <= (others=>'0');  
        else  
            addr <= addrbus;  
        end if;  
  
        if(we='1') then  
            memdata(to_integer(unsigned(addr))) <= databus;  
        end if;  
    end if;  
end process;
```

- 仿真器提示内存读写在下降沿，将上升沿改为下降沿



第三部分

Part One

测试结果


测试结果

- n设为9



```
27 => std_logic_vector(to_unsigned(loop_addr, 8)),  
28 => X"00",  
29 => X"00",  -- total  
30 => X"00",  -- i  
31 => X"09",  -- n  
others => RSNOP
```


测试结果


0、1、3、6、10、15、21、28、36、45之后不变实现了1~9的累加

 




测试结果

  

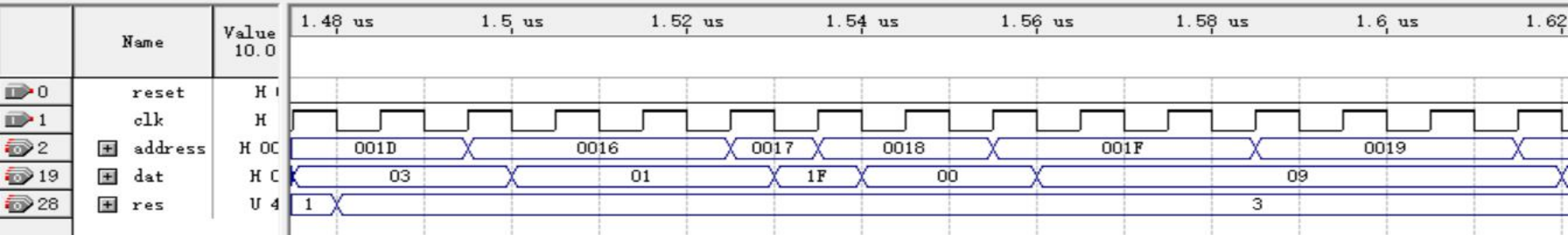Master Time Bar: 10.0 us Pointer: 1.48 us Interval: -8.52 us Start:



测试结果

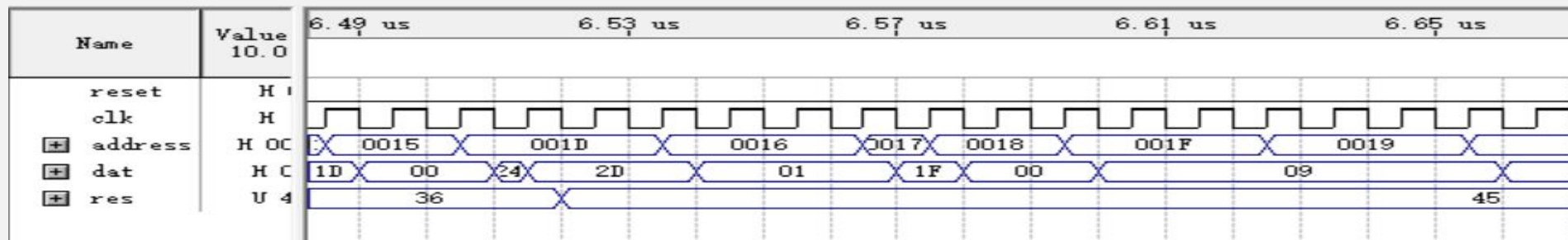 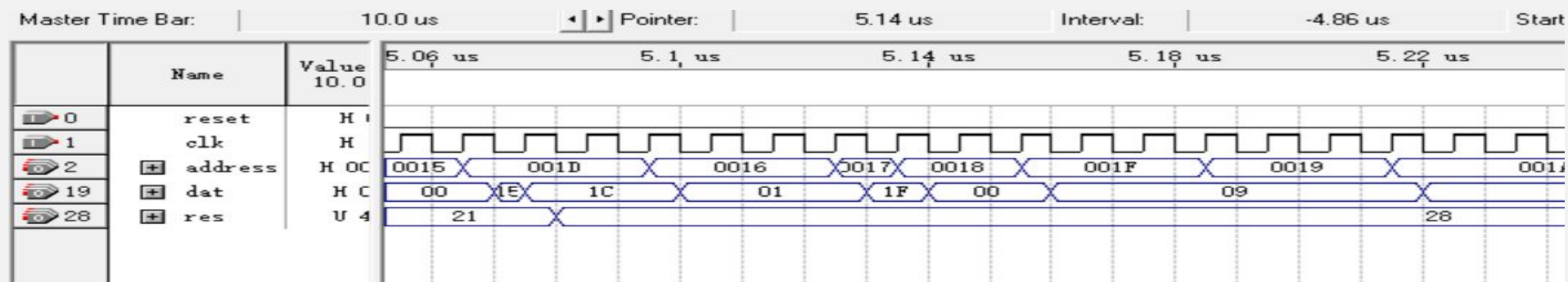



演示完毕 谢谢欣赏